

WIRE MAZE GAME USING ARDUINO

GROUP MEMBERS:

Nihar Ranjan jena – 22EC01001

Vikram Patil – 22EC01008

Aim of the experiment:

To design and implement a wire maze game that detects user contact with the maze wire and keeps track of the number of hits using an arduino.

Objectives:

- Develop a circuit that detects the contact of the key with maze.
- Display the total hit count of the user on LCD screen.
- If the count exceeds the limit then the game is over.
- Alert the user with a buzzer and LED indicator upon contact.
- Provide a way for the user to reset the game and start again.

Working principle:

1. Initialization: Pin 3 is configured as **INPUT_PULLUP** to keep the maze wire at a HIGH state. Pin 2 is set for the **reset button**. Red and Green LEDs (pins 5 and 4), and the buzzer (pin 6) are set as outputs. The **hit count** is initialized to zero, and the **game lost flag** is set to false.

2. Maze Wiring and Contact Detection: One end of the maze wire is connected to pin 3, with the user operating a key to touch the maze. When the key touches the maze wire, a LOW signal is sent to pin 3. Arduino increments the **hit count**, activates the **Red LED**, and sounds the **buzzer**.

3. Game Logic: If the hit count exceeds the limit: The **game lost flag** is set. "YOU LOST" is displayed on the LCD. A continuous buzzer tone signals the loss.

4. Reset Mechanism: The **reset button** on pin 2 resets the game. When pressed, a HIGH signal is sent, resetting the hit count and clearing the game lost flag.

5. Auditory and Visual Feedback: **Buzzer** provides feedback on contact and game loss events. **Red LED** signals hit detection, while the **Green LED** shows no contact. A **White LED** can indicate idle status when no contact is made.

6. User Interaction and Game Play: The **LCD** displays the **hit count** and updates in real time. The system uses **debounce delays** to ensure smooth gameplay and user interaction.

CONNECTIONS:

1. LCD with I2C Module (16x2 LCD): **VCC** → Arduino **5V**, **GND** → Arduino **GND**, **SDA** → Arduino **A4** (Data line for I2C communication), **SCL** → Arduino **A5** (Clock line for I2C communication)

2. Buzzer: **Positive Terminal (+)** → Arduino **Pin 6**, **Negative Terminal (-)** → **GND**

3. LEDs: **Green LED: Anode (long leg)** → Arduino **Pin 4**, **Cathode (short leg)** → **GND** (through a 220Ω resistor).


Red LED: Anode (long leg) → Arduino **Pin 5**, **Cathode (short leg)** → **GND** (through a 220Ω resistor).

4. Wire Maze Input (Game Input): One end of the maze wire → Arduino **Pin 3**, The other end of the maze wire left open.

Pull-up Configuration for Pin 3: Use the internal pull-up resistor by declaring pinMode (wireMazePin, INPUT_PULLUP) in the code. No external resistor is needed unless you face issues with sensitivity, in which case you can add a 10kΩ resistor between **Pin 3** and **5V**.

5. Reset Button: One terminal → Arduino **Pin 2**, Other terminal → **GND**., Configure the internal pull-up resistor in the code with pinMode(resetButtonPin, INPUT_PULLUP).

CIRCUIT DIAGRAM:

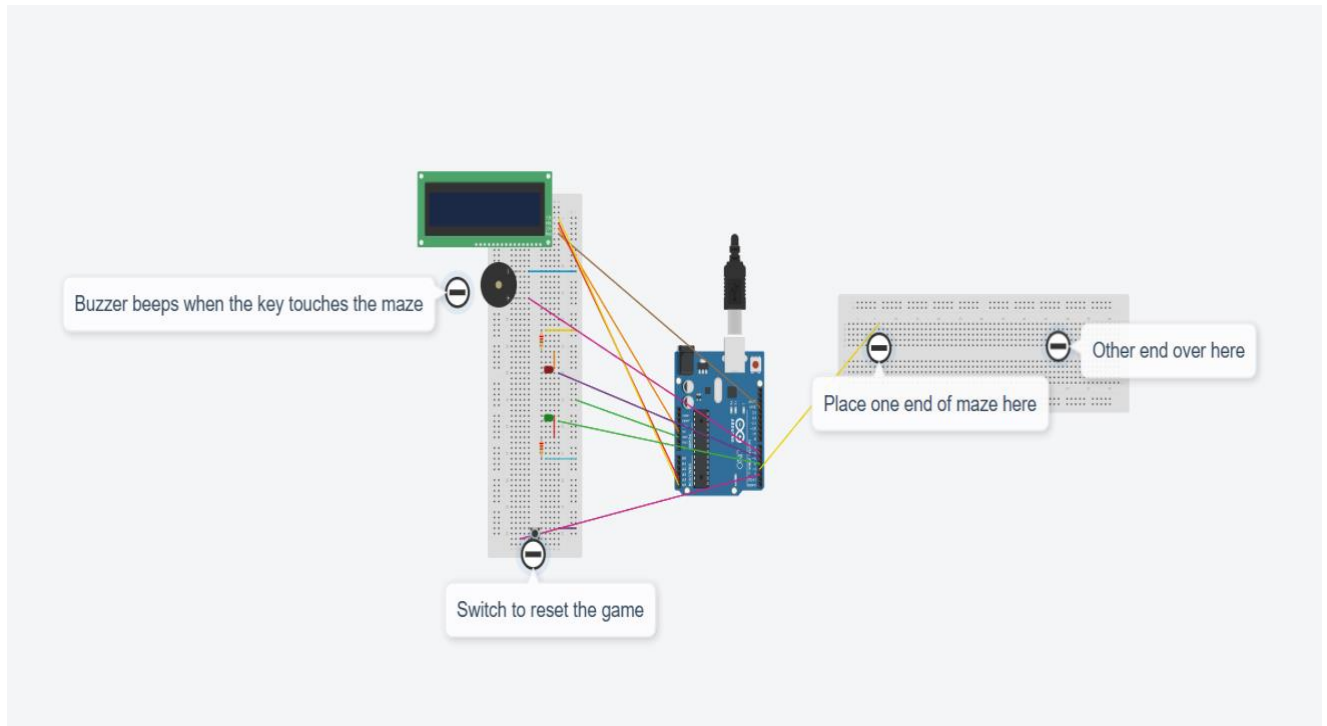

Learnings Outcomes:

- ** We gained practical experience with the fundamentals of serial communication and successfully implemented it during this experiment.
- ** We explored various Arduino IDE commands to perform specific tasks and developed a better understanding of the code flow in the Arduino environment.
- ** We learned about the functionality and working principles of different components, including I2C modules, LCD displays, switches, and buzzers.
- ** We explored the integration of visual and auditory feedback mechanisms using LEDs and a buzzer to enhance user interaction.
- ** We gained insights into implementing conditional logic for real-time decision-making, such as detecting hits and resetting the game state.